


REVIEW OF LOGIC DEVICES

Prepared by :A. B. Modi
Target Audience : 5th Semester Students


LEARNING OBJECTIVES

- ❖ Understand difference between combinational circuits and sequential circuits
- ❖ Understand basic S-R latch
- ❖ Understand different types of flip-flops
- ❖ Buffers and Controlled Buffers
- ❖ Registers
- ❖ Decoders and Encoders

COMBINATIONAL CIRCUITS

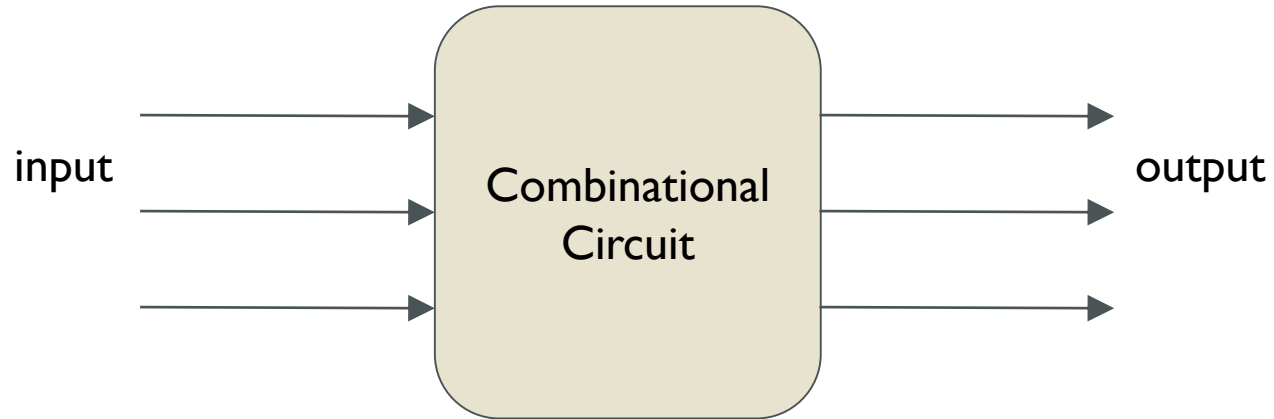

SEQUENTIAL CIRCUITS

 

- It is important that any meaningful circuit, any design, any hardware, any system have to necessarily contain sequential circuits if you want to have a behaviour pattern as per a sequence of events.
- A storage element is required. (Memory)


REQUIREMENT OF MEMORY

- ❖ If stored data is 0, it must remain 0 as long as it is possible.
- ❖ If stored data is 1, it must remain 1 as long as possible.

LATCH

→ A basic storage element is called latch.


Characteristics Table of S-R Latch using NOR Gate			
S	R	Q	\bar{Q}
0	0	Memory (as before)	
0	1	1	0
1	0	0	1
1	1	Not used	

 

S – R Latch using
NOR Gate

LATCH

Characteristics Table of S-R Latch using NAND Gate			
S	R	Q	\bar{Q}
0	0	Not used	
0	1	0	1
1	0	1	0
1	1	memory	

 

S – R Latch using
NAND Gate


FLIP-FLOP

- When clock signal is introduced in Latch, it is called Flip-Flop.
- Clock signal is High
 - ➔ S & R combination will change the output.
- Clock signal is Low
 - ➔ S & R combination will not change the output.
 - ➔ Memory is retained.

S – R FLIP-FLOP

Characteristics Table of S-R Flip-Flop

Clock Signal	S	R	Q	\bar{Q}
0	X	X	Memory	
1	0	0	Memory	
1	0	1	0	1
1	1	0	1	0
1	1	1	Not used	

 


Logic Diagram of S – R Flip-Flop

S – R FLIP-FLOP

Characteristics Table of S-R Flip-Flop


Clock Signal	S	R	Q	\bar{Q}
0	X	X	Memory	
1	0	0	Memory	
1	0	1	0	1
1	1	0	1	0
1	1	1	Not used	

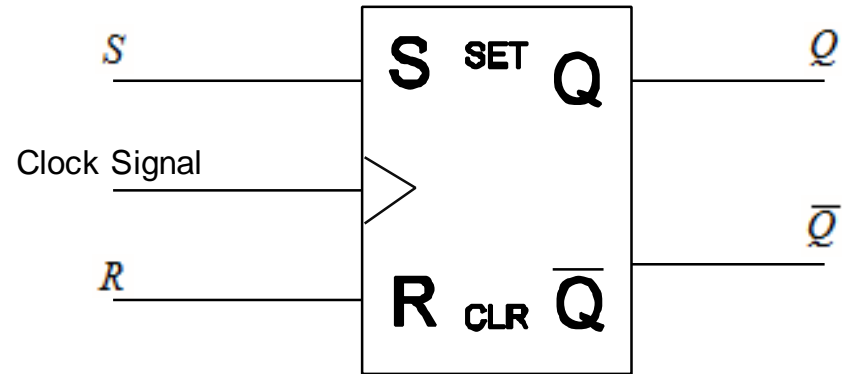



Symbol of S – R Flip-Flop

CLOCK SIGNAL

 - What is Clock Signal ?
- Why do we need this clocking operation ?
- How to decide clock signal length ?



D FLIP-FLOP

 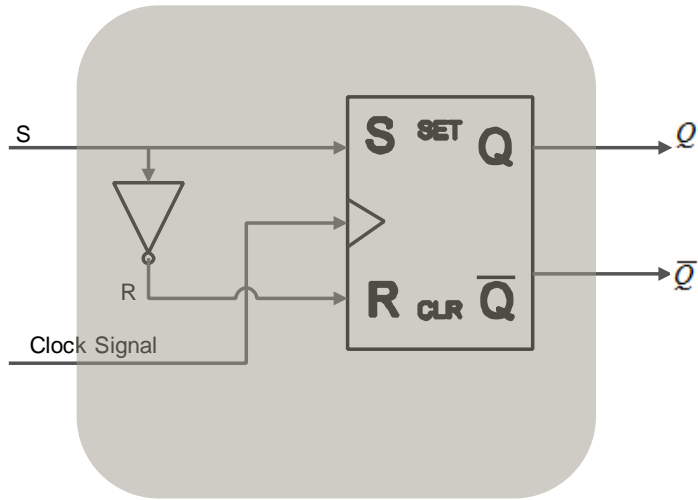

Symbol of D Flip-Flop

D FLIP-FLOP

Characteristics Table of S-R Flip-Flop

Clock Signal	S	R	Q	\bar{Q}
0	X	X	Memory	
1	0	0	Memory	
1	0	1	0	1
1	1	0	1	0
1	1	1	Not used	




Characteristics Table of D Flip-Flop

Clock Signal	S	R	Q	\bar{Q}
0	No change in Data Stored			
1	1	0	1	0
1	0	1	0	1

D FLIP-FLOP

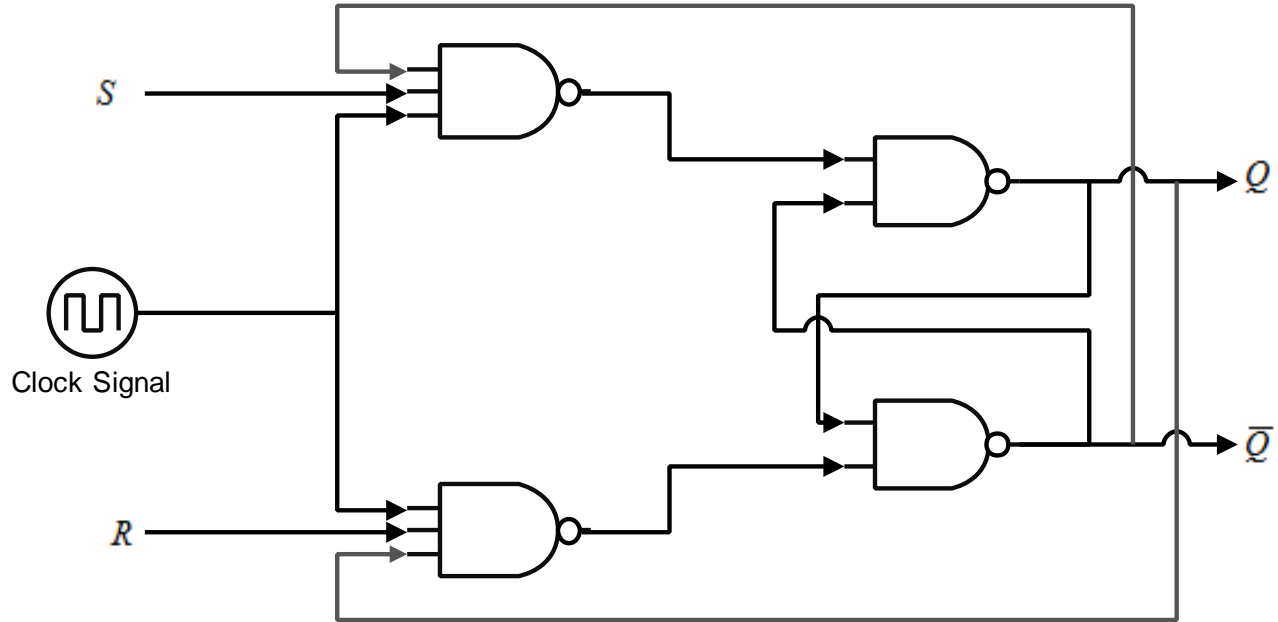- ❖ D Flip-Flop is one bit storage element.
- ❖ Used in Data Storage Device.






Characteristics Table of Flip-Flop				
Clock Signal	S	R	Q	\bar{Q}
1	1	0	1	0
1	0	1	0	1


Characteristics Table of Flip-Flop				
Clock Signal	S	R	Q	\bar{Q}
1	1	1	1	0
			0	1
			1	0
			0	1
			1	0
			0	1
			1	0



Depends on propagation delay of flip-flop




Racing

 

 

  

J-K FLIP-FLOP

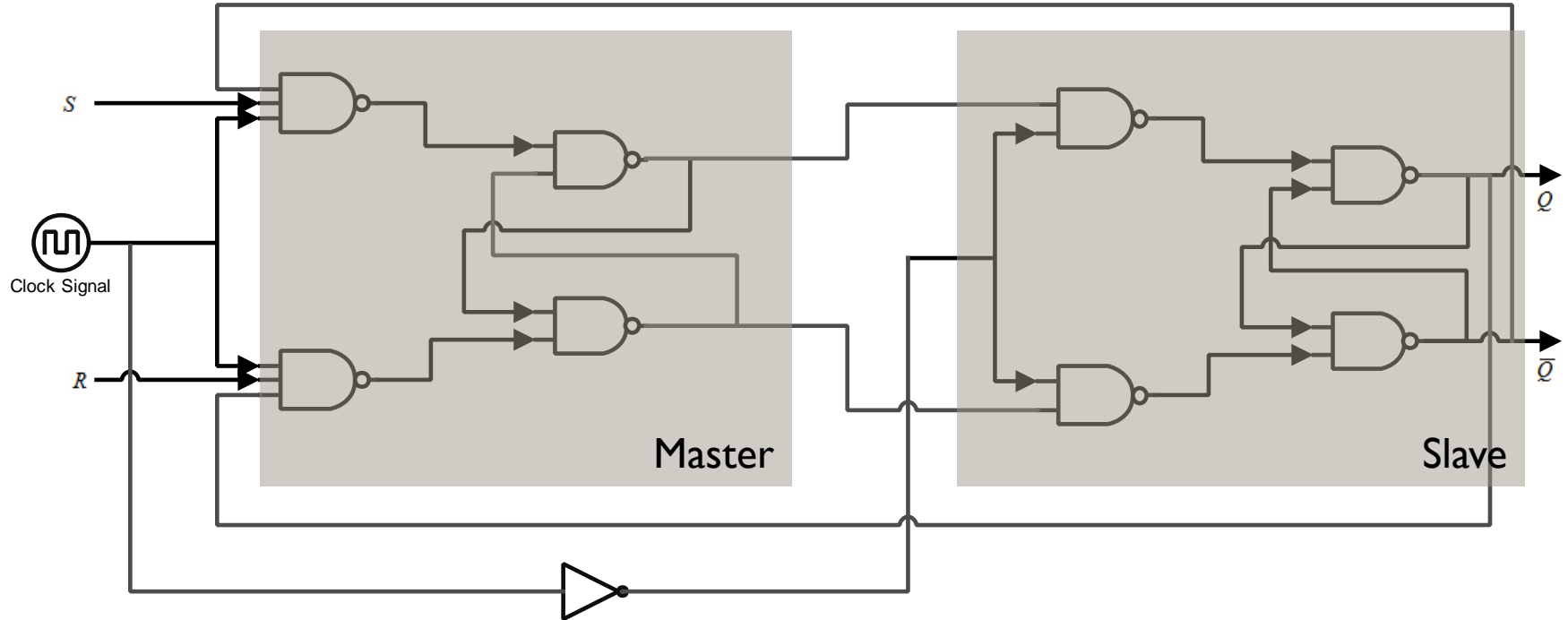


Logic Diagram of J – K Flip-Flop

J-K FLIP-FLOP

Characteristics Table of J-K Flip-Flop


Clock Signal	J	K	Q_n	$\overline{Q_n}$
0	X	X	Memory	
1	0	0	Memory	
1	0	1	0	1
1	1	0	1	0
1	1	1	Q_{n-1}	$\overline{Q_{n-1}}$

 

Symbol of J-K Flip-Flop

T FLIP-FLOP

Characteristics Table of T Flip-Flop		
Clock Signal	T	Q_n
0	X	Q_{n-1}
1	0	Q_{n-1}
1	1	$\overline{Q_{n-1}}$

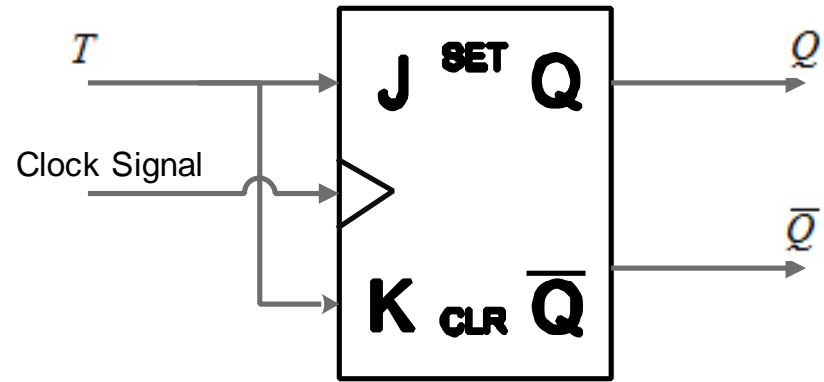

Symbol of T Flip-Flop

EDGE TRIGGERED FLIP-FLOP

- ❖ Level Triggered Flip-Flop
- ❖ Positive Edge Triggered Flip-Flop
- ❖ Negative Edge Triggered Flip-Flop

REQUIRED RESOURCES

- ✓ NPTEL (National Program on Technology Enhanced Learning)
- ✓ Scilab (Open Source Software)
- ✓ Apache Open Office (Open Source Software)
- ✓ Wikipedia (Free Online Encyclopaedia)
- ✓ Google Slides (Open Source Application)
- ✓ Google Drawings (Open Source Application)